



Programme: B.TECH (COMP)/B.TECH (EXTC)/B.TECH (ELECT)/B.TECH (DATA SCI)

Year: I/Semester I (Exam Year: 2024-2025)

Subject: Basic Electrical Engineering and Digital Electronics **Time:** 10:00 am - 12:00 pm (02:00 Hrs.)

Date: 27 Jan 2025


Max Marks: 60

END SEMESTER EXAMINATION ODD SEM-I(2024-2025)

- Instructions: 1. This question paper contains 3 pages
2. Answer to each new question to be started on a fresh page.
3. Figure in right hand side indicates full marks


1. 15

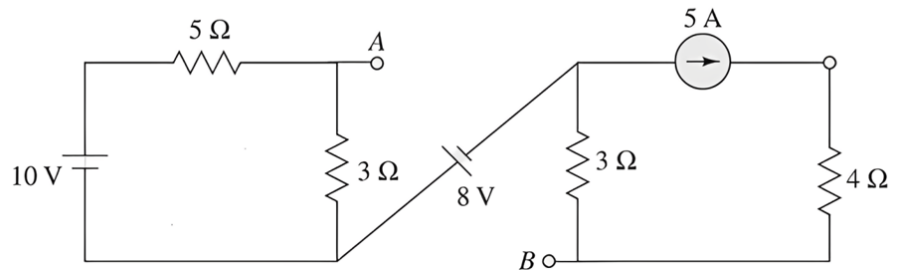- A. 1. Determine the potential difference V_{AB} for the given network




B. 1. 5

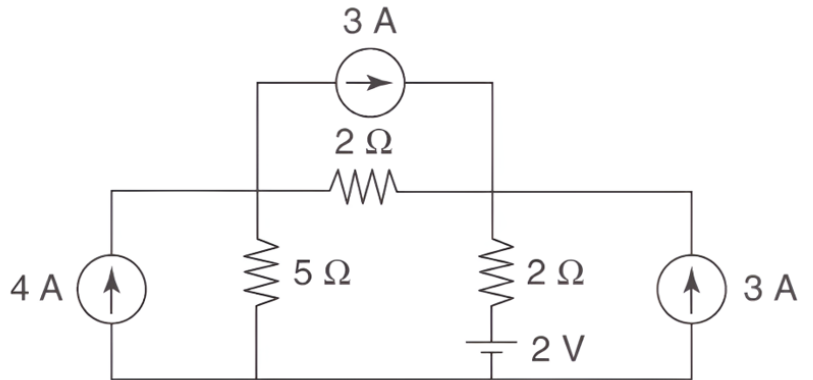- i. Find the current through the 5Ω register in the network using mesh analysis



----- OR -----

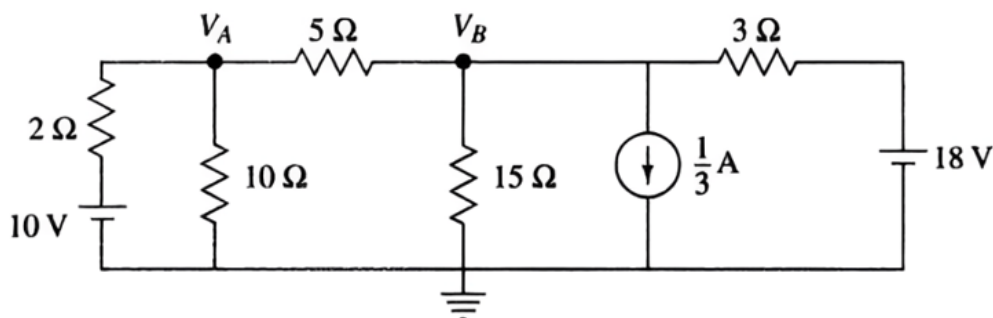- ii. Find V_A and V_B using nodal analysis 5



C. 1. Obtain the sum of three voltages. 5


$$V_1 = 147.3 \cos(\omega t + 98.1^\circ), V_2 = 294.6 \cos(\omega t - 45^\circ), V_3 = 88.4 \sin(\omega t + 135^\circ)$$

2.

15

A. I. Determine the current through 5Ω resistor in the network using Thevenin's theorem.

5

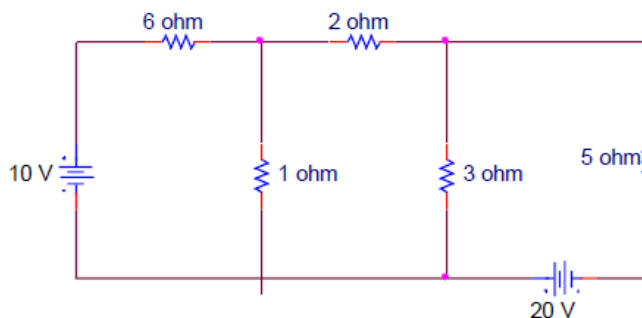


B. I.

10

- i. In the Circuit shown, find the current flowing through 2Ω resistor using Superposition theorem.


10

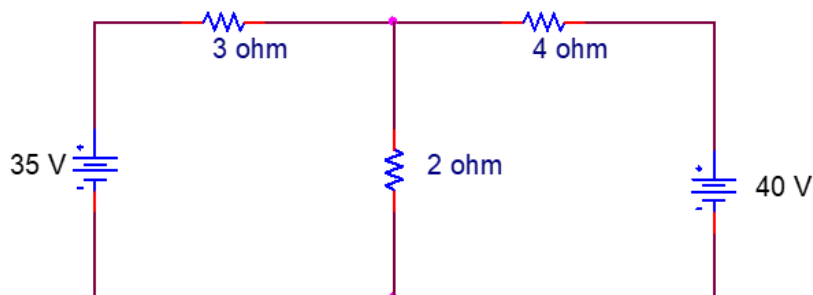

----- OR -----

- ii. Derive the formulae to convert Delta connected network into its equivalent Star connected network. Also find the equivalent resistance between the terminals A and B.

10

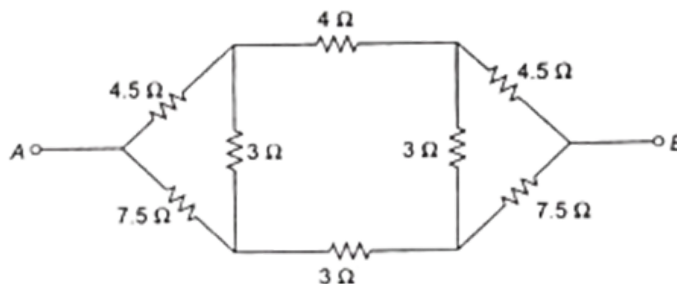

3.

15

A. I.

5

- i. An impedance of $(7 + j5)\Omega$ is connected in parallel with another impedance of $(10 - j8)\Omega$ across a 230 V, 50 Hz supply.

5


Calculate:

- (i) Admittance, conductance and susceptance of the combined circuit, and
(ii) Total current and power factor.

----- OR -----

- ii. Find the RMS value of the waveform shown.

5

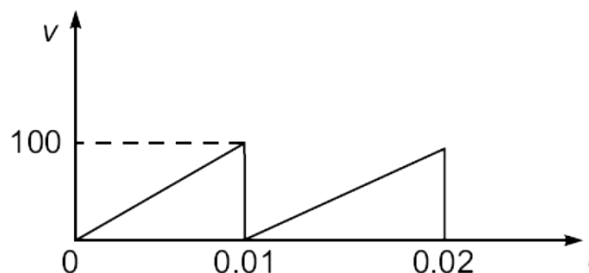

- B. I. A coil having a resistance of 10Ω and an inductance of 40 mH is connected to a 200 V, 50 Hz supply.

10

Calculate: impedance of the coil, current, power factor, power consumed, Reactive Power.

4. 15
- A. I. 5
- i. Perform the following Number system conversions: 5
1. $(1011.111)_2 = (\text{-----})_{10}$
 2. $(105.65)_{10} = (\text{-----})_2$
 3. $(456.37)_8 = (\text{-----})_{16}$
 4. $(BEEDE.AB)_{16} = (\text{-----})_2$
 5. $(253.65)_{10} = (\text{-----})_8$
- ii. Prove the following Boolean expressions: 5
1. $AC + \bar{A}BC = AC + BC$
 2. $AB + ABC + AB(E+F) = AB$
- B. I. What do you mean by Universal gates? Implement NOT, AND and OR gates using only NOR gates. 5
- C. I. 1. Draw neat diagram, write truth table and explain the operation of SR flip-flop. 5