

**Programme:** B.Tech in Electronics & Telecommunication Engineering

**Year: II/Semester III (Exam Year: 2024-2025)**

**Subject:** Electronics Devices & Circuits

**Time:** 09:00 am - 11:00 am (02:00 Hrs.)

**Date:** 09 Dec 2024

**Max Marks:** 60

**END SEMESTER EXAMINATION ODD SEM -III (2024-2025)REGULAR**

- Instructions:
1. This question paper contains 2 pages
  2. Answer to each new question to be started on a fresh page.
  3. Figure in right hand side indicates full marks
  4. Draw neat diagrams wherever required.
  5. Assume suitable data if required.

1.

15

A. For the biasing circuit shown in fig.1.b Determine the  $I_C$ ,  $V_{CE}$ ,  $V_C$ ,  $V_B$  and  $V_E$ .

Transistor parameters are:  $V_{BE}=0.7V$ , and  $\beta=120$ .

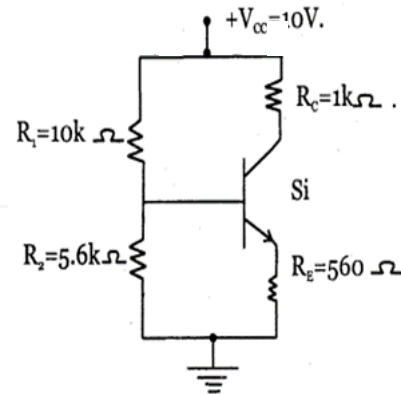


fig.1.b

10

B. .

5

- i. What is biasing? Why there is a need of biasing? Also explain what are the factors affecting stability of the transistor.

5

----- OR -----

- ii. For a voltage divider biasing circuit,  $\beta = 100$ ,  $R_B=370K$  and  $R_E=2K$ . Determine the stability Factor.

5

2.

15

A. Draw and explain high frequency model for BJT in CE configuration.


5

B. .

10


- i. Draw a small signal equivalent circuit of the given circuit in fig. and derive the expression for voltage gain, input impedance and output impedance.

10

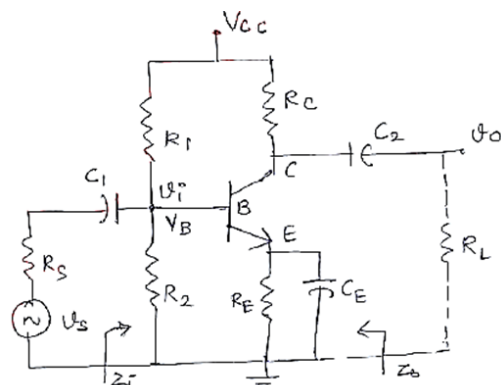

----- OR -----

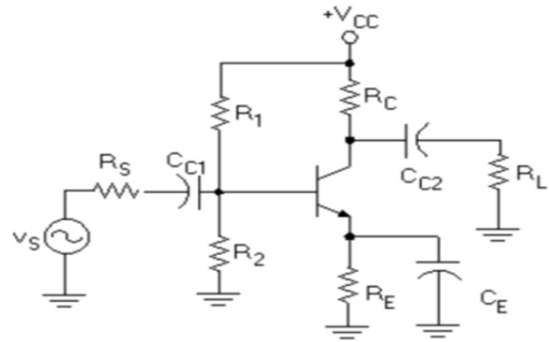- ii. Derive the equation for Lower cutoff frequency FL due to coupling capacitors and bypass capacitors for the CE amplifier circuit shown below. also find expression for midband voltage gain.



3.


A. What are the various topologies of negative feedback amplifiers? Discuss any one in detail.

B. .

- i. Draw and explain the construction and working of N-Channel Depletion type MOSFET in detail with transfer and drain current characteristics.

----- OR -----

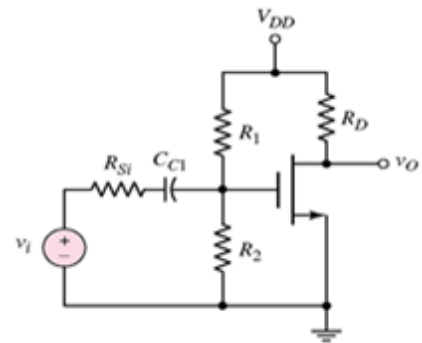- ii. For the MOSFET common source amplifier shown in fig. below, analyze and derive the expression for voltage gain and input impedance.



4.

A. Draw and explain Hartley oscillator using BJT.

B. .

- i. Derive an expression for maximum power efficiency of a Class B Push pull Power amplifier.

----- OR -----

- ii. Differentiate between Voltage amplifier and power amplifier.